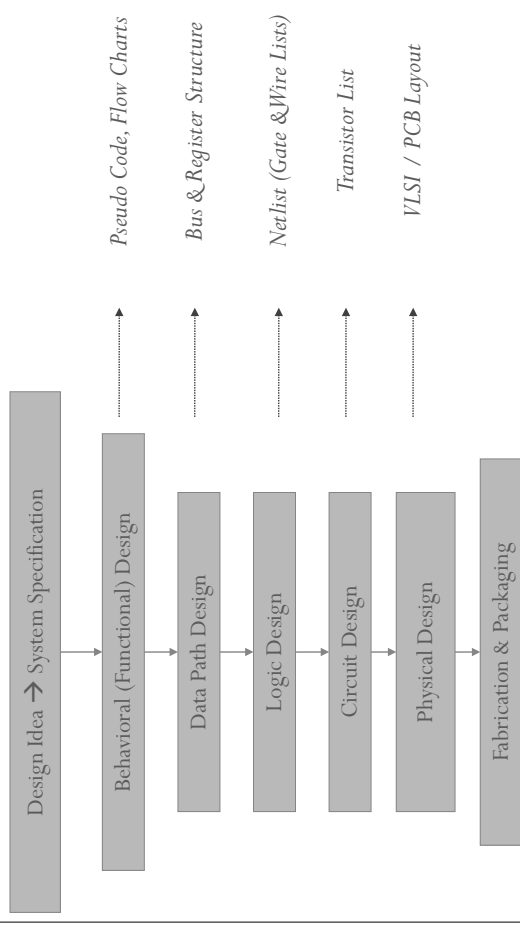


HARDWARE DESCRIPTION LANGUAGES

- HDL are used to describe the hardware for the purpose of modeling, simulation, testing, design, and documentation.
- Modeling: behavior, flow of data, structure
- Simulation: verification and test
- Design: synthesis

Digital System Design Cycle



Purpose of VHDL

- Problem
 - Need a method to quickly design, implement, test, and document increasingly complex digital systems
 - Schematics and Boolean equations inadequate for million-gate IC
- Solution
 - A hardware description language (HDL) to express the design
 - Associated computer-aided design (CAD) or electronic design automation (EDA) tools for synthesis and simulation
 - Programmable logic devices for rapid implementation of hardware
 - Custom VLSI application specific integrated circuit (ASIC) devices for low-cost mass production

Design Automation & CAD Tools

- Design Entry (Description) Tools
 - Schematic Capture
 - Hardware Description Language (HDL)
- Simulation (Design Verification) Tools
 - Simulators (Logic level, Transistor Level, High Language Level "HLL")
- Synthesis Tools
- Test Vector Generation Tools

VHDL: Why to use?

- **Reasons to use VHDL**
 - Power and flexibility
 - Device-independent design
 - Portability among tools and devices
 - Device and tool benchmarking capability
 - VLSI ASIC migration
 - Quick time-to-market and low cost (with programmable logic)
- **Problems with VHDL**
 - Loss of control with gate-level implementation (so what?)
 - Inefficient logic implementations via synthesis (engineer-dependent)
 - Variations in synthesis quality among tools(always improving)

History of VHDL

- Two widely-used HDLs today
- VHDL
- Verilog HDL (from Cadence, now IEEE standard)
- VHDL - VHSIC Hardware Description Language



Very High Speed
Integrated Circuit


Design Flow in VHDL

- Define the design requirements
- Describe the design in VHDL
 - Top-down, hierarchical design approach
 - Code optimized for synthesis or simulation
- Simulate the VHDL source code
 - Early problem detection before synthesis
- Synthesize, optimize, and (place and route) the design for a device
 - Synthesize to equations and/or netlist
 - Optimize equations and logic blocks subject to constraints
 - Fit into the components blocks of a given device
- Simulate the post-layout design model
 - Check final functionality and worst-case timing
- Program the device (if PLD) or send data to ASIC vendor


▪ VHDL history

- Created by DOD to document military designs for portability
- IEEE standard 1076 (VHDL) in 1987
- Revised IEEE standard 1076 (VHDL) in 1993
- IEEE standard 1164 (object types standard) in 1993
- IEEE standard 1076.3 (synthesis standard) in 1996

Digital System Design Cycle

 


Design Tool Flow (1)

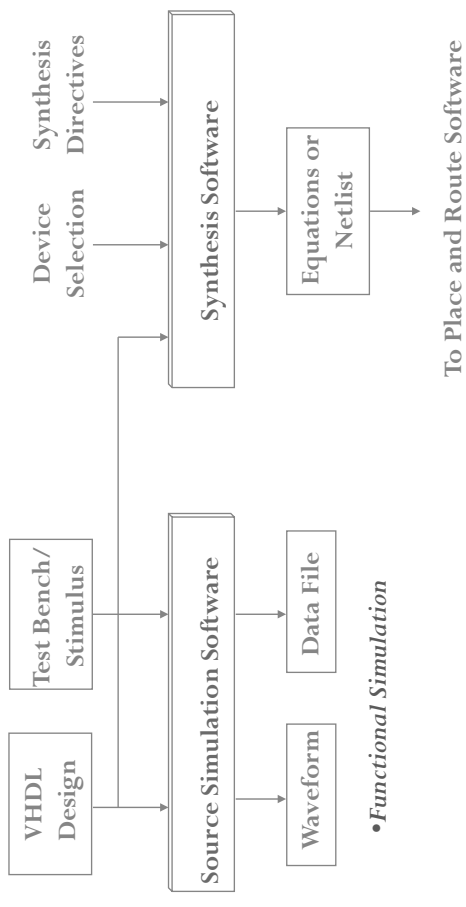

STYLES in VHDL


- **Levels of Abstraction (Architectural Styles):**
 - Behavioral
 - High level, algorithmic, sequential execution
 - Hard to synthesize well
 - Easy to write and understand (like high-level language code)
 - **Dataflow**
 - Medium level, register-to-register transfers, concurrent execution
 - Easy to synthesize well
 - Harder to write and understand (like assembly code)
 - **Structural**
 - Low level, netlist, component instantiations and wiring
 - Trivial to synthesize
 - Hardest to write and understand (very detailed and low level)

• Design Tool Flow (2)

 

An Interface Description for the Full Adder
 
```
entity full_adder is
  port(
    X, Y, Cin: in bit;    -- input ports
    Sum, Cout: out bit);  -- output ports
end full_adder;
```



Introduction to VHDL



A First Example


Basic Building Blocks of VHDL Descriptions

Structural Description in VHDL


Data Flow Description in VHDL

Behavioral Description in VHDL

Views of the Full Adder

 

A Full Adder

 

A Structural Architecture

architecture structure_view of full_adder is

```

component half_adder
  port (
    I1, I2: in bit; -- inputs
    Carry: out bit; -- outputs
    Sum: out bit);
end component;
component or_gate
  port (
    I1, I2: in bit;
    O: out bit);
end component;
signal a, b, c: bit;
begin
  U1: half_adder port map ( X, Y, a, b);
  U2: half_adder port map ( b, Cin, c, Sum);
  U3: or_gate port map (a, c, Cout);
end structure_view;
```


Boolean Equations for the Full Adder

$$S = X \oplus Y$$

$$\text{Sum} = S \oplus C_{\text{in}}$$


$$C_{\text{out}} = XY + SC_{\text{in}}$$

A Structure for the Full Adder

 

a, b, and c are intermediate nodes

The Design Entity Concept

 

...and any one of a collection of alternative architectures.

A Behavioral Architecture

```
architecture behavioral_view of full_adder is
begin
    process
        variable N: integer;
        constant sum_vector: bit_vector (0 to 3) := "0101";
        constant carry_vector: bit_vector (0 to 3) := "0011";
    begin
        N := 0;
        if X = '1' then N := N+1; end if;
        if Y = '1' then N := N+1; end if;
        if Cin = '1' then N := N+1; end if;
        Sum <= sum_vector (N) after 20 ns;
        Cout <= carry_vector (N) after 30 ns;
        wait on X, Y, Cin;
    end process;
end behavioral_view;
```

A Dataflow Architecture

```
architecture dataflow_view of full_adder is
    signal S: bit;
begin
    S <= X xor Y after 10 ns;
    Sum <= S xor Cin after 10 ns;
    Cout <= (X and Y) or (S and Cin) after 20 ns;
end dataflow_view;
```

Combining Styles of Description

```
architecture mixed_view of full_adder is
    component xor_gate
        port ( I1, I2: in bit;
              O: out bit);
    end component;
    signal S: bit;
begin
    V1: Cout <= (X and Y) or (S and Cin) after 20 ns;
    V2: xor_gate port map ( X, Y, S);
    V3: xor_gate port map ( S, Cin, Sum);
end mixed_view;
```

Function Table for the Full Adder

Inputs			Outputs		
Cin	X	Y	Cout	Sum	
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	
1	0	0	0	1	
1	0	1	1	0	
1	1	0	1	0	
1	1	1	1	1	

A Configuration Declaration for the Full Adder

```


configuration alpha of full_adder is
  for structure_view
    for U1, U2: half_adder use
      entity work.half_add (macro4950),
    end for;
    for U3: or_gate use
      entity work.or2 (cell2396);
    end for;
  end for;
end alpha;

```


Characteristics of the Design Hierarchy

- A complete design consists of a hierarchy of interconnected design entities.
- Each design entity consists of an *entity declaration* and any one of the associated *architecture declarations*.
- All communication between design entities takes place through their interfaces.
- A design entity makes no assumptions about the context in which it is used.
- The replacement of one architecture by another (with the same functionality) will have no external effect.

Design Space of VHDL

 

The Design Library

 


Objects

- **Objects** are containers of values. There are four classes of objects in VHDL: constants, variables, files and signals.
- **Constants** have a single value that may not be changed.
- **Variables** have a single value which can be changed by assignment.
- **Files** contain sequences of values that can be read or written.
- **Signals** have a past history of values, a present value, and set of projected future values; only future values can be changed by assignment.
- All objects are of some *type*.

Types

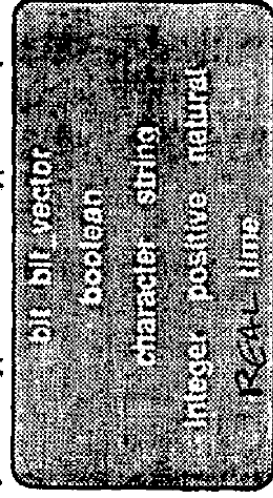- A type is a set of values.
- The type of each object is *static*; it cannot be changed during simulation.
- The type of an object determines how it can be used; for example, only certain operators are defined for a type.
- Several commonly used types and subtypes are predefined:



- The user may construct additional types using the predefined types as **building blocks**.

Introduction to VHDL

A First Example



Basic Building Blocks of VHDL Descriptions

Structural Description in VHDL

Data Flow Description in VHDL

Behavioral Description in VHDL

Lexical Elements

Identifiers

COUNT
aBc
X
1123
VHDL
VH_DL
ABC

Decimal literals

12
0
1E6
123_456
3.141_593

Physical literals

10 ns
2.2 v
50 pI

Character literals

'A'
'a'
'G'
'y'
'.'

String literals

"Hold time out of range"
"A"
"@#\$%+!"
"state "ready"" enter"
"111100001111"


Based literals

2#110_1010#
16#CA#
16#1.fff#e+2

Bit string literals

X"FOF"
B"111_100_001_111"
O"7417"

Operations

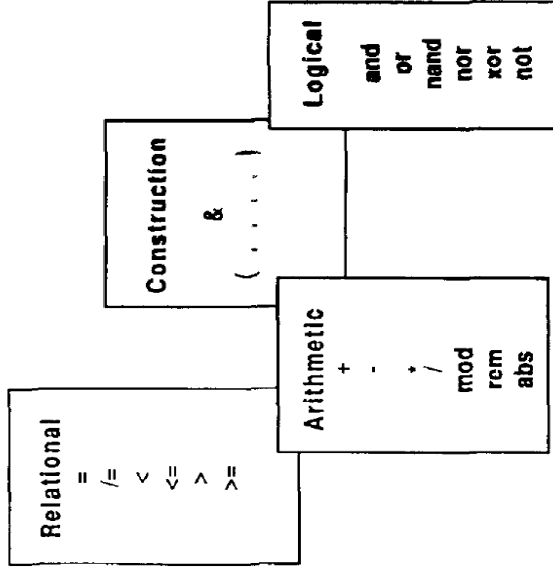

Examples of Types and Objects

```

type tri_value is ('0', '1', 'Z');
type system_state is (idle, test, target, fire, evaluate);
type small_integer is range 0 to 9;
type small_real is range 0.0 to 1.0;
type int_sequence is file of integer;

signal a, b, c: bit := '0';
signal stable: tri_value;

constant mid_range: small_integer := 5;

variable counter: small_integer;
variable random_number: small_real;

file counts: int_sequence is "project/data/rom243";

```

Expressions

Arithmetic	$(-b + \sqrt{b^2 - 4.0 \cdot a \cdot c}) / (2.0 \cdot a)$
Construction	operation & register & base & displacement (day => WED, date => (July, 4, 1776))
Relational	delay <= 30 ns name > "Jones" event.date = (November, 12, 1984)
Logical	CLOCK and not RESET (A_reg xor memory_data) and B_reg (A = '1' and B = '0') or (C = '0' and B = '1')

Examples of Types and Objects

```

type digit_display is array (1 to 20) of small_integer;
signal target_count: digit_display;

type state_descriptor is record
  state: system_state;
  sensors: bit_vector (1 to 16);
  operational: boolean;
end record;
type state_history is array (integer range <=>) of state_descriptor;
variable R234_history: state_history (0 to 2047);
.
.
.
R234_history (J) := (test, X"F0FC", false);
.
.
.

```

Sequential Statements

```

Nfact := 1;
fact: for j in 2 to N loop
    Nfact := Nfact * j;
end loop fact;

case DAY
    when SAT | SUN => staff := 3;
    when MON | FRI => staff := 5;
    when TUE to THU => staff := 10;
end case;

while register(31) = '0' loop
    register := left_shift (register);
end loop;

if abs (A - B) < delta then
    delta := delta/2.0;
elsif A-B > 0.0 then
    guess := guess + delta;
else
    guess := guess - delta;
end if;

loop
    wait for 20 ms;
    locate (target, distance);
    exit when distance < 0.25 km;
    range(target) := distance;
end loop;

```

Statements

- Statements specify the organization and operation of a design.
- **Sequential statements** specify algorithms (step by step instructions).
- **Concurrent statements** specify
 - Component interconnections
 - Hierarchical structure
 - Regular structure
 - Data flow or register transfer operations
- Sequential statements are encapsulated in processes and subprograms for use in concurrent contexts.

Concurrent Statements

- The **structure** of a design is specified using
 - Component instantiation statements
 - Generate statements
 - Block statements
- The **behavior** of a design is specified using
 - Concurrent signal assignment statements
 - Process statements
 - Concurrent procedure calls
 - Concurrent assertions

Sequential Statements

- Similar to those in any high-level programming language:
 - If and case statements
 - Loop statements
 - Procedure call and return statements
 - Variable assignment statement
 - Null statement
- Unique to VHDL:
 - Signal assignment statement
 - Wait statement
 - Assertion statement

An Example of a Package

```
package tristate is
```

```
type MVL is ('0', '1', 'Z', 'E');
function "and" (X, Y: MVL) return MVL;
function "or" (X, Y: MVL) return MVL;
function "not" (X: MVL) return MVL;

type MVL_vector is array (integer range <=>) of MVL;
function tri_resolve (sources: MVL_vector) return MVL;
type tri_vector is array (integer range <=>) of tri_resolve MVL;
subtype byte is tri_vector (7 downto 0);
```

```
constant high_Z: byte;
function "and" (X, Y: tri_vector) return tri_vector;
function "or" (X, Y: tri_vector) return tri_vector;
function "not" (X: tri_vector) return tri_vector;
```

```
end tristate;
```

An Example of a Package

```
package body tristate is
  constant high_Z: byte := "ZZZZZZZZ";
  function "and" (X, Y: MVL) return MVL is
    .
    .
    .
  end "and";

  function "or" (X, Y: MVL) return MVL is
    .
    .
    .
  end "or";
  .
  .
  .
end tristate;
```

Concurrent Statements

```
S1 <= D1 after 10 ns, '0' after 30 ns;
```

```
S2 <=
  X after 10 ns when C1 = '0' else
  Y after 7.5 ns when C2 = '0' else
  Z after 5 ns;
```

```
delay_line: for K in 1 to N generate
  S(K) <= S(K-1) after 100 fs;
end generate;
S(0) <= X after 100 fs;
```

```
with transmit_quality select
  channel <= source when good,
             source - 2v when avera
             0.0v when poor;
```

```
parity: -- inputs X, Y, Z; output Result.
block
  signal a: bit;
begin
  a <= X xor Y after 5 ns;
  Result <= a xor Z after 5 ns;
end parity;
```

Library Units

entity

Describes the interface with the outside world and any common characteristics of all implementations of a device.

architecture body

Describes the organization or operation of a device.

configuration

Selects design entities from a design library for component instances within an architecture.

package

Encapsulates a set of related declarations.

package body

Defines the bodies of subprograms and the values of deferred constants declared in a package.

Interface to the System

```

use tristate.all;
entity micro_system (
  DATA: inout byte;
  ADDR: inout bit_vector (11 downto 0);
  INT: in bit;
  RW: inout bit;
  IOREQ: out bit )
end micro_system;

```

Introduction to VHDL

A First Example

Basic Building Blocks of VHDL Descriptions

Structural Description in VHDL

Data Flow Description in VHDL

Behavioral Description in VHDL




Components of the System

```

use tristate.all;
package parts is
  component clock
    port (C: out bit);
  end component;
  component ROM
    port ( DATA: out byte; ADDR: in bit_vector (11 downto 0);
          CS1, CS2: in bit );
  end component;
  component RAM
    port ( DATA: inout byte; ADDR: in bit_vector (11 downto 0);
          CS1, CS2, RW: in bit );
  end component;
  component decoder
    port ( P: in bit_vector (1 to 2); SOUT: out bit_vector (1 to 4));
  end component;
  component processor
    port ( DATA: inout byte; ADDR: out bit_vector (11 downto 0);
          CLOCK, INT: in bit; MEMREQ, RW: out bit; IOREQ: out bit );
  end component;
end parts;

```

Simple Microprocessor System

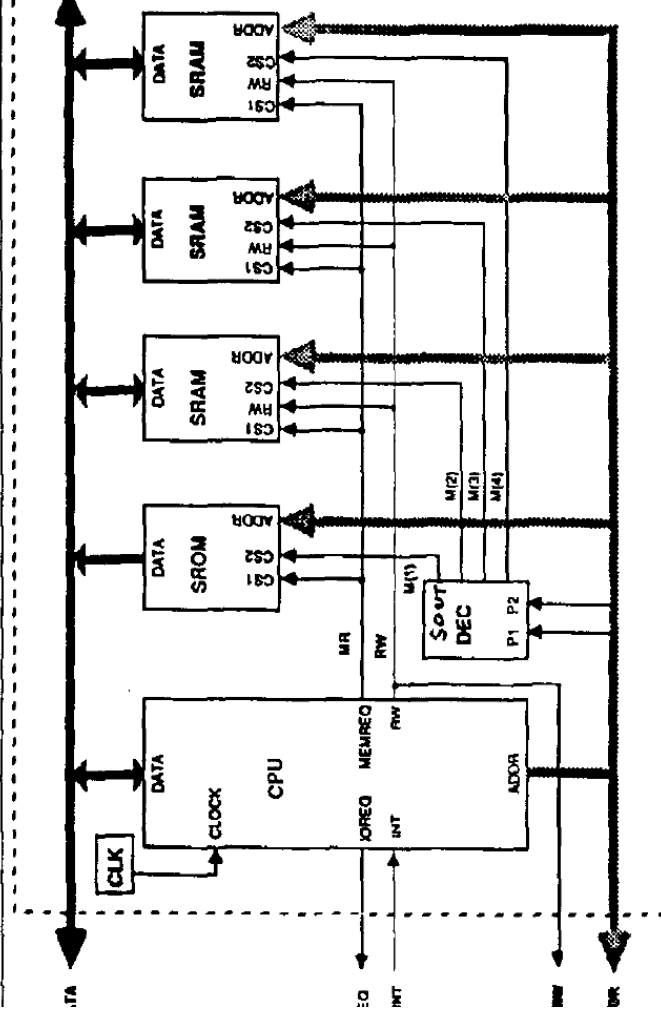

Component Instantiation

Component Declarations

- A **component instance** is created by a **component instantiation statement**.
- Each instance is a new copy of the component, unrelated to any other instance.
- Each instance identifies the signal that is attached to each port of the component.
- Unused ports may be left unconnected.

- A **component declaration** defines the interface to a subcomponent of a design.
- The declaration specifies:
 - The name of the component
 - The names and types of its ports
 - The direction in which data flows through each port

Uses of Component Instantiation

- The designer can postpone decisions about the behavior of portions of his design during top-down decomposition.
- The designer can reuse a portion of a design that has already been created and stored in a design library.
- The design can choose either structural or functional decomposition.

Structural Architecture for the System

```
use parts.all;
architecture build1 of micro_system is
    signal CL, MR: bit;
    signal M: bit_vector (1 to 4);
begin
    CPU: processor port map (DATA, ADDR, CL, INT, MR, RW, IOREQ);
    DEC: decoder port map (P(1) => ADDR (11), P(2) => ADDR (10), M);
    CLK: clock port map (CL);
    SRAM: ROM port map (DATA, ADDR (9 downto 0), MR, M(1));
    RAM_array:
        for i in 2 to 4 generate
            SRAM: RAM port map (DATA, ADDR (9 downto 0), MR, M(i), RW);
        end generate;
end build1;
```

Introduction to VHDL

A First Example

Basic Building Blocks of VHDL Descriptions

Structural Description in VHDL

Data Flow Description in VHDL


Behavioral Description in VHDL



A Configuration of the System

```
library CMOS_A, CMOS_mem;
configuration simple of build1 is
  for micro_system
    for CPU: processor use
      entity CMOS_A.micro_processor (UP2400);
    end for;
  for DEC: decoder use
    entity CMOS_A.one_of_four (C0901);
  end for;
  for CLK: clock use
    entity CMOS_A.clock (C2310);
  end for;
  for SROM: ROM use
    entity CMOS_mem.ROM_1K8 (functional);
  end for;
  for RAM_array
    for SRAM(2 to 4): RAM use
      entity CMOS_mem.RAM_1K8 (functional);
    end for;
  end for;
end simple;
```

General Model of Functional Devices

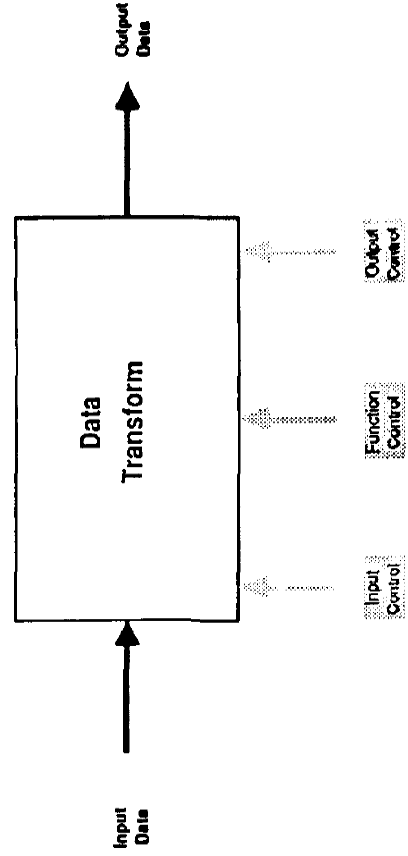


Binding Instances to Library Units

- A design system may support any number of *design libraries*.
- Each component instance must be *bound* to an entity in some design library with a *configuration specification*.
- An *explicit* configuration specification can appear in a configuration declaration, or right after the declaration of a component.
- If no explicit configuration specification for an instance appears, then the *default* configuration specification takes effect.

Tracing Signal Assignment Execution

A <= B or C after 5 ns;

 

Unconditional Signal Assignment

- The *simple signal assignment* models a data transform in which all inputs are data inputs:


S <= intval (J) after 5 ns, abs K after 10 ns, (L+M)/2 after 15 ns;

- The **target** to the left of the arrow will receive the values defined by the **waveform** on the right.
- Each **waveform element** has a value part and a delay part.
- The value is any expression of the same type as the target.
- The delay is an expression of the physical type TIME. If the after clause is missing, a delay of 0 is assumed.
- All signals used in value parts are defined to be inputs.

Uses of Simple Signal Assignment

- Modeling combinational circuits:


parity <= A xor B xor C xor D;

 

- Modeling asynchronous sequential circuits:

Q <= S nand Q;

QB <= R nand Q;

 

Signal Assignment Execution

- A signal assignment statement executes in response to changes on its input signals.
- Each value in the waveform will be scheduled to appear on the target after the specified delay.
- If the assignment statement executes again, previously scheduled values may be **overridden**.
- A delay of zero represents an infinitesimally small delay – signal assignment never takes effect immediately.

Uses of Conditional Signal Assignment

- To switch between two functions based on a single condition:

```
RegC <= RegA after 150 ns when A_enable else RegB after 150 ns;
```

- To switch among functions when multiple control lines must be considered in some order of precedence:


```
bus_cycle <=
  dma when dma_req else
  interrupt when interrupt_req and not interrupt_inhibit else
  sync when ext_sync else
  instruction;
```

Selected Signal Assignment

- A single expression selects which of several transforms is to be applied:

```
with opcode select
  result <=
    A and B when and_op,
    A or B when or_op,
    A xor B when xor_op,
    not A when not_op;
```

 - The expression is evaluated when any input changes.
- The waveform associated with the value is assigned to the target.
- Every possible value of the expression must have a corresponding waveform.



Conditional Signal Assignment

- A series of conditions controls which of several functional transforms drives the target:

```
count <=
  3 when A='1' and B='1' else
  2 when A='1' else
  1 when B='1' else
  0;
```

- When any input changes, the conditions are evaluated in order.
- The waveform associated with the first true condition is assigned to the target.
- The last waveform must not have a condition – it is the default.

Modeling a Latch

- A device with input control can be modeled with a guarded block.

```

latch: block (load_enable = '1')
begin
  data <= guarded Dbus;
end block latch;
    
```

Uses of Selected Signal Assignment

- Selected signal assignment models multiplexors, selectors and similar devices:

SM: with system_state select
next_state <=

target when idle | test,
fire when target,
evaluate when fire,
idle when evaluate;

DEC: with P1 & P2 select

SOUT <=


"1000" after 12 ns when "00",

"0100" after 12 ns when "01",


"0010" after 12 ns when "10",

"0001" after 12 ns when "11";

Latch Timing

 

Input Control

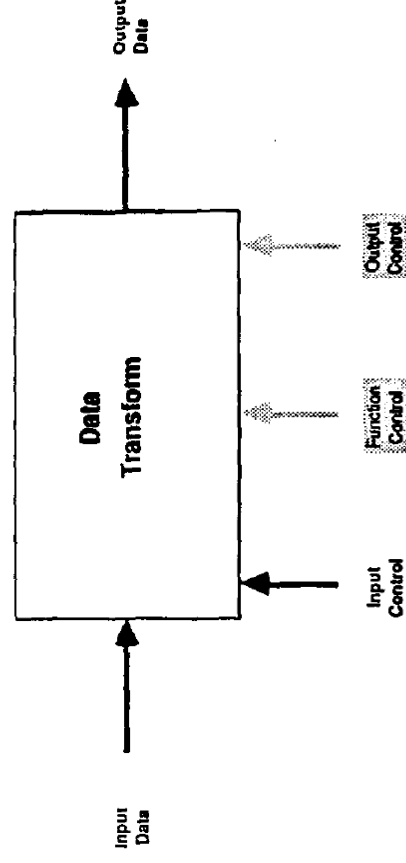

Modeling the Shift Register

```


shifter:
block (SH = '1' and rising (CLK))
  signal v: bit_vector (1 to 4); -- represents internal storage of register
begin
  with LR & S1 & S2 select
    v <= guarded
      Q & v(1) & v(2) & v(3) when "000",
      '0' & v(1) & v(2) & v(3) when "001",
      '1' & v(1) & v(2) & v(3) when "010",
      v(4) & v(1) & v(2) & v(3) when "011",
      v(2) & v(3) & v(4) & Q when "100",
      v(2) & v(3) & v(4) & '0' when "101",
      v(2) & v(3) & v(4) & '1' when "110",
      v(2) & v(3) & v(4) & v(1) when "111";
  output <= v after 10 ns;
end block shifter;

```

Signal GUARD

- A block statement may have a *guard expression* .
- A block statement with a guard expression implicitly declares a signal named **GUARD**.
- The value of **GUARD** is always updated to the current value of the guard expression.
- Guarded signal assignments implicitly reference signal **GUARD**.
- Signal **GUARD** may also be explicitly referenced like any other signal.

Output Control

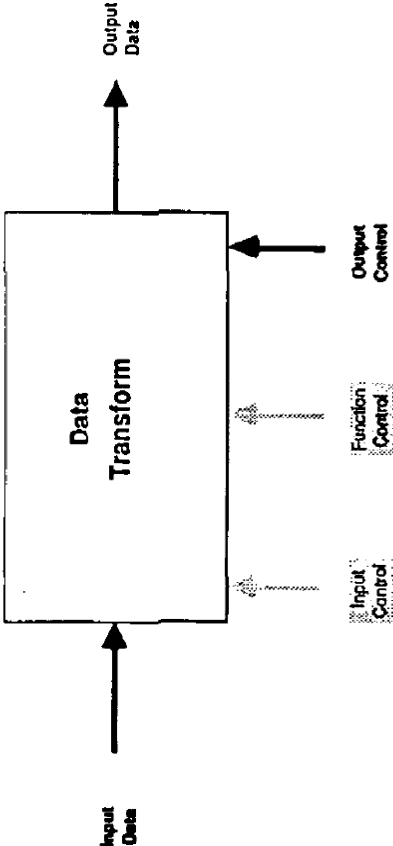


A Synchronous Serial-Input Shift Register

CLK	SH	LR	S1	S2	A	B	C	D
0	X	X	X	X	v(1)	v(2)	v(3)	v(4)
R	0	X	X	X	v(1)	v(2)	v(3)	v(4)
	1	0	0	0	Q*	v(1)	v(2)	v(3)
	0	0	0	1	0	v(1)	v(2)	v(3)
	0	1	0	0	1	v(1)	v(2)	v(3)
	0	1	1	1	v(4)	v(1)	v(2)	v(3)
	1	0	0	0	v(2)	v(3)	v(4)	Q*
	0	1	0	1	v(2)	v(3)	v(4)	0
	1	1	1	0	v(2)	v(3)	v(4)	1
	1	1	1	1	v(2)	v(3)	v(4)	v(1)

*Q : serial input

One Signal with Multiple Sources

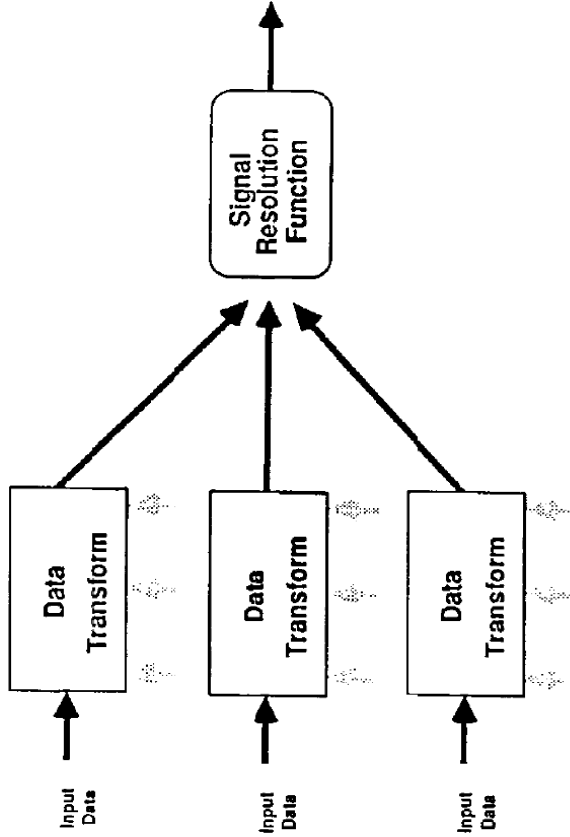

Modeling Output Disconnection

- Tristate outputs can effectively disconnect from the circuits they drive.
- Output disconnection can be modeled indirectly by defining a data type that includes a value meaning "not driving":

```
type MVL is ('0', '1', 'Z', 'E');
```

Signal Resolution

```
package tristate is
    .
    .
    .
    type MVL_vector is array (integer range <>) of MVL;
    function tri_resolve (sources: MVL_vector) return MVL;
    type tri_vector is array (integer range <>) of tri_resolve MVL;
    .
    .
    .
end package tristate;
```

Using a "Not Driving" Value

```
signal common: tri_vector (0 to 7);
signal A_data, B_data, C_data, D_data: tri_vector (0 to 7);
signal A_enable, B_enable, C_enable, D_enable: MVL;
.
.
.
U1: common <= A_data when A_enable = '1' else "ZZZZZZZZ";
U2: block (load = '1')
    signal tmp: tri_vector (0 to 7);
    begin
        tmp <= guarded B_data;
        common <= tmp when B_enable = '1' else "ZZZZZZZZ";
    end block U2;
U3: with C_enable & D_enable select
    common <=
        C_data when "10",
        D_data when "01",
        C_data or D_data when "11",
        "ZZZZZZZZ" when "00";
```

Summary

- Concurrent signal assignment provides data flow and register transfer level descriptive styles.
- Function control is modeled with conditional and selected signal assignment.
- Input control is modeled with guard expressions and guarded assignment.
- Output control can be modeled by using appropriate data types in conjunction with signal assignment statements.

Signal Resolution

```
package body tristate is
.
.
.
function tri_resolve (sources: MVL_vector) return MVL is
variable resolved_value: MVL := 'Z';
begin
  for i in sources'range loop
    if resolved_value = 'Z' then
      resolved_value := sources(i);
    elsif sources(i) /= 'Z'
      return 'E';
    end if;
  end loop;
  return resolved_value;
end tri_resolve;
.
.
end package tristate;
```

Introduction to VHDL

Using a "Not Driving" Value

```
signal common: tri_vector (0 to 7);
signal A_data, B_data, C_data, D_data: tri_vector (0 to 7);
signal A_enable, B_enable, C_enable, D_enable: MVL;
.
.
.
U1: common <= A_data when A_enable = '1' else "ZZZZZZZZ";

U2: block (load = '1')
  signal tmp: tri_vector (0 to 7);
begin
  tmp <= guarded B_data;
  common <= tmp when B_enable = '1' else "ZZZZZZZZ";
end block U2;

U3: with C_enable & D_enable select
  common <=
    C_data when "10",
    D_data when "01",
    C_data or D_data when "11",
    "ZZZZZZZZ" when "00";
```


A First Example

Basic Building Blocks of VHDL Descriptions

Structural Description in VHDL

Data Flow Description in VHDL

Behavioral Description in VHDL

 

Behavioral Architecture of the RAM

```

architecture behavioral of RAM_1K8 is
begin
    process
        subtype matrix_item is tri_vector (7 downto 0);
        type matrix is array (0 to 1023) of matrix_item;
        variable memory: matrix;
    begin
        while CS1 and CS2 = '1' loop
            case RW is
                when '0' => DATA <= memory(intval(ADDR)) after 70ns;
                when '1' => memory(intval(ADDR)) := DATA;
            end case;
            wait on CS1, CS2, DATA, ADDR, RW;
        end loop;
        DATA <= "ZZZZZZZZ" after 55 ns;
        wait on CS1, CS2;
    end process;
end behavioral;

```

Modeling Complex Behavior

- Concurrent signal assignment statements model simple devices whose outputs are always a function of their inputs.
- A more general capability is required to model devices with internal (hidden) state information.
- A technique is required to describe device behavior in algorithmic (sequential) terms.
- The *process statement* provides a compact representation for arbitrary deterministic behavior.
- The *subprogram* encapsulates a sequence of sequential statements.

A Package for Byte Objects

```

use work.tristate.all;
package byte_objects is
    type byte_vector is array (natural range <>) of byte;
    type byte_sequence is file of byte;
    function read_bytes (file_name: string; length: natural) return byte_vector;
end byte_objects;

package body byte_objects is
    function read_bytes (file_name: string; length: natural) return byte_vector is
        file data: byte_sequence is in file_name;
        variable elements: byte_vector ( 0 to length-1);
    begin
        for i in elements'range loop
            read (data, elements (i));
        end for;
        return elements;
    end read_bytes;
end byte_objects;

```

Modeling A Random Access Memory

```

use work.tristate.all;
entity RAM_1K8 (
    DATA: inout tri_vector;
    ADDR: bit_vector;
    CS1, CS2: bit;
    RW: bit)
end RAM_1K8;

```

Behavioral Description

- Processes are concurrent statements; function calls appear in expressions; procedure calls are sequential statements.
- Processes and subprograms contain:
 - Declarations of constants, variables, subprograms, etc.
 - Sequential statements specifying how output values are computed.
- The description contains no information about the implementation of a device.

Files

- A *file type definition*
 - Gives the file type a name
 - Specifies what sort of objects it contains
 - Implicitly declares READ and WRITE procedures
- A *file declaration*
 - Creates an object of some file type
 - Associates the object with an external file
 - Specifies whether the file is to be read or written

More, More, More!

- Generic parameters
- Guarded signals
- Libraries and configuration
- Global signals
- User defined attributes
- Assertion of operating conditions and characteristics
- The VHDL type model
- Signals, events and the simulation cycle
- Modeling methods

A Self-Initializing ROM

```
use work.tristate.all, work.byte_objects.all;
entity ROM_1K8
  port ( DATA: out byte; ADDR: in bit_vector (9 downto 0);
        CS1, CS2: in bit);
end ROM_1K8;

use work.twos_comp.all;
architecture functional of ROM_1K8 is
  constant address_bits: integer := 10;
  constant file_name: string := "SYS$LOGIN:\JON.DATA\JR1234";
  constant ROM_contents: byte_vector :=
    read_bytes (file_name, 2**address_bits);
begin
  DATA <= ROM_contents (intval ( ADDR)) when CS1&CS2 = "11"
    else high_Z;
end functional;
```