

## Pre-synthesis Simulation

- Simulation for design validation
  - Done before a design is synthesized
  - Referred to as RT level, or Pre-synthesis Simulation
  - The Required Test data: generated graphically using waveform editors, or through a testbench
- RTL level Simulation is clock accurate
  - The advantage is speed over gates/transistor-level
- Outputs of simulators:
  - Waveforms (for visual inspection)
  - Text for large designs for machine processing

## Testbench in Verilog

- Generates test data and observes simulation results
  - Tests of a designed system functionality
  - Detects incompatibility of design component
- Testbench is a Verilog module that uses Verilog high-level constructs for:
  - Data Generation
  - Response Monitoring
  - Handshaking with the design
  - Each testbench instantiates a design module

## Pre-synthesis Simulation

- **Actual hardware behaves differently than RTL model.**
  - Timing and delays of the parts used,
    - Nonzero delay between clock edges.
    - Output is unpredictable if the clock frequency applied is too fast for propagation delays.
- **This is typical of a pre-synthesis or high-level behavioral simulation.**
  - Potential timing problems of the hardware that are due to gate delays cannot be detected.

## Design Validation

- An important task in any digital system design
- The process to check the design for any design flaws
- A design flaw due to:
  - Ambiguous Problem Specifications
  - Designer Errors
  - Incorrect Use of Parts in the Design
- Can be done by:
  - Simulation
  - Assertion Verification
  - Formal Verification

# Structural vs Behavioral Models


- Structural model
  - Just specifies primitive gates and wires
  - i.e., the structure of a logical netlist
- Behavioral model
  - More like a procedure in a programming language
  - Still specify a module in Verilog with inputs and outputs...
  - ...but inside the module you write code to tell what you want to have happen, NOT what gates to connect to make it happen
  - i.e., you specify the behavior you want, not the structure to do it
- Why use behavioral models
  - For testbench modules to test structural designs
  - For high-level specs to drive logic synthesis tools

# Assertion Verification

- **Assertion Monitors:** Used to continuously check for design properties during simulation
  - Assertion Monitors developed to assert that the Design Properties are not violated
  - Firing of an assertion verification: alerts the malfunctioning of design according to the designer's expectation
  - Instead of having to inspect simulation results manually or by developing sophisticated test benches.
- **Design Properties:** Certain conditions have to be met for the design to function correctly
- **Open verification library (OVL):** provides a set of assertion monitors for monitoring common design properties
 
# Representation: Structural Models

- Structural models
  - Are built from gate primitives and/or other modules
  - They describe the circuit using logic gates — much as you would see in an implementation of a circuit.
    - You could describe your lab1 circuit this way
- Identify:
  - Gate instances, wire names, delay from a or b to f.



# Formal Verification

- **Formal verification:** The process of checking a design against certain properties
  - Examining the design to make sure that the described properties by the designer to reflect correct behavior of the design hold under all conditions
- **Property's Counter Examples:** Input combinations that causes a property to fail
- **Property coverage:** Measures how much the design is exercised by the property

## Four-Valued Logic

- Logic with multi-level logic values
  - Logic with these four values make sense
    - Nand anything with a 0, and you get a 1. This includes having an x or z on the other input. That's the nature of the nand gate
    - Nand two x's and you get an x
- Note: z treated as an x on input. Their rows and columns are the same
- If you forget to connect an input ... it will be seen as an x.
- At the start of simulation, everything is an x.

		Input B			
Nand	Input A	0	1	x	z
		0	1	1	1
	1	1	0	x	x
	x	1	1	x	x
	z	1	1	x	x

A 4-valued truth table for a Nand gate with two inputs

## How to build and test a module

- Construct a “test bench” for your design
  - Develop your hierarchical system within a module that has input and output ports (called “design” here)
- Develop a separate module to generate tests for the module (“test”)
- Connect these together within another module (“testbench”)


```
module testbench ();
  wire  l, m, n;
  design d (l, m, n);
  test  t (l, m);
  initial begin
    //monitor and display
    ...
  end
endmodule
```

```
module design (a, b, c);
  input  a, b;
  output c;
  ...
endmodule

module test (q, r);
  output q, r;
  initial begin
    //drive the outputs with signals
    ...
  end
endmodule
```
 
## Representation: Gate-Level Models

- Need to model the gate's:
  - Function
  - Delay
- Function
  - Generally, HDLs have built-in gate-level primitives
  - Verilog has NAND, NOR, AND, OR, XOR, XNOR, BUF, NOT, and some others
  - The gates operate on input values producing an output value
    - typical Verilog gate instantiation is:



## Four-Valued Logic

- Verilog Logic Values**
  - The underlying data representation allows for any bit to have one of four values
    - 1, 0, x (unknown), z (high impedance)
    - x — one of: 1, 0, z, or in the state of change
    - z — the high impedance output of a tri-state gate.
- What basis do these have in reality?**
  - 0, 1 ... no question
  - z ... A tri-state gate drives either a zero or one on its output. If it's not doing that, its output is high impedance (z). Tri-state gates are real devices and z is a real electrical affect.
  - x ... not a real value. There is no real gate that drives an x on to a x is used as a debugging aid. x means the simulator can't determine the answer and so maybe you should worry!
- BTW ...**
  - some simulators keep track of more values than these. Verilog will in some situations.

## The test module (Test generator)

- \$monitor
  - prints its string when executed.
  - after that, the string is printed when one of the listed values changes.
  - only one monitor can be active at any time
  - prints at end of current Simulation time
- Function of this tester
  - at time zero, print values and set a=b=0
  - after 10 time units, set b=1
  - after another 10, set a=1
  - after another 10 set b=0
  - then another 10 and finish

```
module testHalfAdd(a, b, sum, cOut);
  Input  sum, cOut;
  output a, b;
  reg   a, b;
  initial begin
    $monitor ($time,, "a=%b, b=%b,
      sum=%b, cOut=%b", a, b, sum,
      cOut);
    a = 0; b = 0;
    #10 b = 1;
    #10 a = 1;
    #10 b = 0;
    #10 $finish;
  end
end
```

## More than modeling hardware

- \$monitor — give it a list of variables. When one of them changes, it prints the information. Can only have one of these active at a time. e.g. ...

```
$monitor ($time,, "a=%b, b=%b, sum=%b, cOut=%b", a, b, sum, cOut);
```

Extra commas  
prints spaces


%b is binary, %h hex,  
%d for decimal

```
$display ($time,, "a=%b, b=%b, sum=%b, cOut=%b", a, b, sum, cOut);
```

\$display() — sort of like printf()

## Verilog Design

- Three Verilog modules

 


```
module testbench;
  Wire su, co, a, b;
  halfAdd    U1 (su,co,a,b);
  testHalfAdd U2 (a,b,su,co)
Endmodule
```

```
module testHalfAdd(a, b, sum, cOut);
  Input  sum, cOut;
  output a, b;
  reg   a, b;
  initial begin
    $monitor ($time,, "a=%b, b=%b, sum=%b, cOut=%b",
      a, b, sum, cOut);
    a = 0; b = 0;
    #10 b = 1;
    #10 a = 1;
    #10 b = 0;
    #10 $finish;
  end
endmodule
```

```
module halfAdd (sum, cOut, a, b);
  output sum, cOut;
  Input a, b;
  xor #2 G1(sum,a,b);
  and #2 G2(Count,a,b);
endmodule
```

## Two initial statements?

 

- Things to note
  - Which initial statement starts first?
  - What are the values of `a`, `b`, and `out` when the simulation starts?
  - These appear to be executing concurrently (at the same time). Are they?

## Structural vs Behavioral Models

- Structural model
  - Just specifies primitive gates and wires
  - i.e., the structure of a logical netlist
- Behavioral model
  - More like a procedure in a programming language
  - Still specify a module in Verilog with inputs and outputs...
  - ...but inside the module you write code to tell what you want to have happen, NOT what gates to connect to make it happen
  - i.e., you specify the behavior you want, not the structure to do it
- Why use behavioral models
  - For testbench modules to test structural designs
  - For high-level specs to drive logic synthesis tools

## How do behavioral models fit in?

- How do they work with the event list and scheduler?
  - Initial (and always) begin executing at time 0 in arbitrary order
  - They execute until they come to a “#delay” operator
  - They then suspend, putting themselves in the event list 10 time units in the future (for the case at the right)
  - At 10 time units in the future, they resume executing where they left off.

```

module testHalfAdd(a, b, sum, cOut);
Input  sum, cOut;
output a, b;
reg    a, b;
initial begin
    $monitor ($time,, "a=%b, b=%b,
sum=%b, cOut=%b", a, b,
sum, cOut);
    a = 0; b = 0;
    #10 b = 1;
    #10 a = 1;
    #10 b = 0;
    #10 $finish;
end

```