

```

module busdriver (busin, bushigh, buslow, enh, enl);
input [15:0] busin;
output [7:0] bushigh, buslow;
input enh, enl;
    driver busar3(busin[15:12], bushigh[7:4], enh);
    driver busar2 (busin[11:8], bushigh[3:0], enh);
    driver busar1(busin[7:4], buslow[7:4], enl);
    driver busar0(busin[3:0], buslow[3:0], enl);
endmodule

module busdriver_equiv (busin, bushigh, buslow, enh, enl);
input [15:0] busin;
output [7:0] bushigh, buslow;
input enh, enl;
    driver busar[3:0] (.out({bushigh, buslow}), .in(busin),.en{enh, enh,enl,enl}));
endmodule

```

```

module driver (in, out, en);
input [3:0] in;
output [3:0] out;
input en;
    buff0 ar[3:0] (out, in, en); // array of three-state buffers
endmodule

module driver_equiv (in, out, en);
input [3:0] in;
output [3:0] out;
input en;
    buff0 ar3 (out[3], in[3], en); // each buffer declared separately
    buff0 ar2 (out[2], in[2], en);
    buff0 ar1 (out[1], in[1], en);
    buff0 ar0 (out[0], in[0], en);
endmodule

```

and	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

or	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x

xor	0	1	x	z
0	0	1	x	x
1	1	0	x	x
x	x	x	x	x
z	x	x	x	x

nand	0	1	x	z
0	1	1	1	1
1	1	0	x	x
x	1	x	x	x
z	1	x	x	x

nor	0	1	x	z
0	1	0	x	x
1	0	0	0	0
x	x	0	x	x
z	x	0	x	x

xnor	0	1	x	z
0	1	0	x	x
1	0	1	x	x
x	x	x	x	x
z	x	x	x	x

and X1 (out, a,b);

buf	
input	output
0	0
1	1
x	x
z	x


not	
input	output
0	1
1	0
x	x
z	x

buf b1 X1(z,i);

```

module dffn (q, d, clk);
parameter bits = 1;
input [bits-1:0] d;
output [bits-1:0] q;
input clk ;
    DFF dff[bits-1:0] (q, d, clk); // create a row of D flip-flops
endmodule
module MxN_pipeline (in, out, clk);
parameter M = 3, N = 4;
// M=width,N=depth
input [M-1:0] in;
output [M-1:0] out;
input clk;
wire [M*(N-1):1] t;
// #(M) redefines the bits parameter for dffn
// create p[1:N] columns of dffn rows (pipeline)
dffn #(M) p[1:N] ({out, t}, {t, in}, clk);
endmodule


```

 

Bidirectional pass switches: tran, tranif0, tranif1, rtran, rtranif0, rtranif1;

tranif1 t1 (inout1,inout2,control);

cmos and rcmos

 

cmos (w, datain, ncontrol, pcontrol);

nmos (w, datain, ncontrol);

pmos (w, datain, pcontrol);

pullup, pulldown;

pullup (strong1) p1 (neta), p2 (netb);

bufif1 X1 (outw, inw, control);

bufif0	CONTROL				bufif1	CONTROL							
		0	1	x		z		0	1	x	z		
D		0	0	z	L	L	D		0	z	0	L	L
A		1	1	z	H	H	A		1	z	1	H	H
T		x	x	z	x	x	T		x	z	x	x	x
A		z	x	z	x	x	A		z	z	x	x	x


notif0	CONTROL				notif1	CONTROL						
		0	1	x		z		0	1	x	z	
		0	1	z		H		0	z	1	H	H
D		0	1	z <td>H<td>D</td><td></td><td>0</td><td>z<td>1<td>H<td>H</td></td></td></td></td>	H <td>D</td> <td></td> <td>0</td> <td>z<td>1<td>H<td>H</td></td></td></td>	D		0	z <td>1<td>H<td>H</td></td></td>	1 <td>H<td>H</td></td>	H <td>H</td>	H
A		1	0	z <td>L<td>A</td><td></td><td>1</td><td>z<td>0</td><td>L<td>L</td></td></td></td>	L <td>A</td> <td></td> <td>1</td> <td>z<td>0</td><td>L<td>L</td></td></td>	A		1	z <td>0</td> <td>L<td>L</td></td>	0	L <td>L</td>	L
T		x	x	z <td>x<td>T</td><td></td><td>x</td><td>z<td>x<td>x<td>x</td></td></td></td></td>	x <td>T</td> <td></td> <td>x</td> <td>z<td>x<td>x<td>x</td></td></td></td>	T		x	z <td>x<td>x<td>x</td></td></td>	x <td>x<td>x</td></td>	x <td>x</td>	x
A		z	x	z <td>x<td>A</td><td></td><td>z</td><td>z<td>x<td>x<td>x</td></td></td></td></td>	x <td>A</td> <td></td> <td>z</td> <td>z<td>x<td>x<td>x</td></td></td></td>	A		z	z <td>x<td>x<td>x</td></td></td>	x <td>x<td>x</td></td>	x <td>x</td>	x

pmos rpmos	CONTROL			
		0	1	x z
D		0	0 z	L L
A		1	1 z	H H
T		x	x z	x x
A		z	z z	z z

nmos rnmos	CONTROL				
		0	1	x	z
D	0	z	0	L	L
A	1	z	1	H	H
T	x	z	x	x	x
A	z	z	z	z	z


pmos p1 (out, data, control);

 unidirectional: cmos, nmos, pmos, rcmos, rpmos



strength0										strength1							
7	6	5	4	3	2	1	0	0	1	2	3	4	5	6	7		
Su0	St0	Pu0	La0	We0	Me0	Sm0	HiZ0	HiZ1	Sm1	Me1	We1	La1	Pu1	St1	Su1		

Figure 7-5—Weak x signal strength

 

strength0										strength1							
7	6	5	4	3	2	1	0	0	1	2	3	4	5	6	7		
Su0	St0	Pu0	La0	We0	Me0	Sm0	HiZ0	HiZ1	Sm1	Me1	We1	La1	Pu1	St1	Su1		



H range

—Strength levels for scalar net signal values


Strength name	Strength level
supply0	7
strong0	6
pull0	5
large0	4
weak0	3
medium0	2
small0	1
highz0	0
highz1	0
small1	1
medium1	2
weak1	3
large1	4
pull1	5
strong1	6
supply1	7

strength0										strength1							
7	6	5	4	3	2	1	0	0	1	2	3	4	5	6	7		
Su0	St0	Pu0	La0	We0	Me0	Sm0	HiZ0	HiZ1	Sm1	Me1	We1	La1	Pu1	St1	Su1		

Scale Strength

  

L range

 

Unknown signal range

Wired logic: trand, wand, prior, wor

strength0										strength1						
7	6	5	4	3	2	1	0	0	1	2	3	4	5	6	7	
Su0	St0	Pu0	La0	We0	Me0	Sm0	Hi0	HiZ	Sm1	Me1	We1	La1	Pu1	St1	Su1	

strength0										strength1						
7	6	5	4	3	2	1	0	0	1	2	3	4	5	6	7	
Su0	St0	Pu0	La0	We0	Me0	Sm0	Hi0	HiZ	Sm1	Me1	We1	La1	Pu1	St1	Su1	

wired AND logic value result: 0
wired OR logic value result: 1

Input strength	Reduced strength
Supply drive	Pull drive
Strong drive	Pull drive
Pull drive	Weak drive
Large capacitor	Medium capacitor
Weak drive	Medium capacitor
Medium capacitor	Small capacitor
Small capacitor	Small capacitor
High impedance	High impedance

Strength reduction rules